

Experiment No. 05

Name of the Experiment: Verification of Ohm's Law.

OBJECTIVE:

To verify the following two equivalent forms of Ohm's Law:

- a. Express I as a function of V and R .
- b. Express V as a function of I and R .

THEORY:

Ohm's law describes mathematically how voltage ' V ', current ' I ' and resistance ' R ' in a circuit are related. According to this law:

"The current in a circuit is directly proportional to the applied voltage and inversely proportional to the circuit resistance".

Formula for voltage:

For a constant value of R , V is directly proportional to I

$$\text{i.e. } V = IR$$

Formula for current:

For a constant value of V , I is inversely proportional to R

$$\text{i.e. } I = V/R$$

EQUIPMENTS:

- Variable DC power supply -1piece.
- Digital multimeter (DMM)/ Analog multimeter-1piece.
- Resistances: $1K\Omega$, $2.2K\Omega$, $3.3K\Omega$, $4.7K\Omega$, $5.6K\Omega$, $10K\Omega$ -1piece each.
- Trainer Board.
- Connecting Wires.

Physics Laboratory

CIRCUIT DIAGRAM:

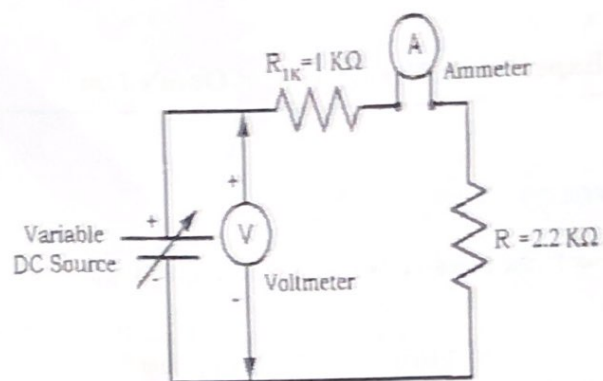


Figure 1: Verification of Ohm's Law

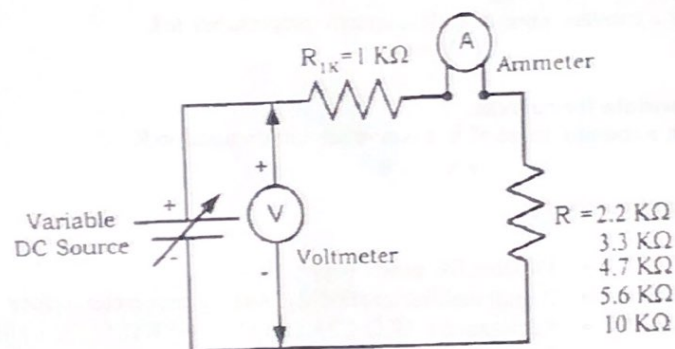


Figure 2 : Verification of Ohm's Law

Physics Laboratory

PROCEDURES:

Current versus voltage:

- Find out the individual resistances by using Ohmmeter and place the value in Table 1. Measure the resistances by constructing a series circuit which is the equivalent resistance from the circuit.
- Construct the circuit of Figure 1. Do not switch on the power supply.
- Turn on the power supply and adjust it to 5V by using Voltmeter. Measure the current I by ammeter and record it in the Table 2.
- Increase the values of voltage as shown in the Table 2. Measure the current I in turn and record the values in Table 2.
- Calculate the values of current I by using $I=V/R_T$. Use measured values of resistances.

Current versus resistance:

- Construct the circuit of Figure 2. Do not switch on the power supply.
- Turn on the power supply and adjust it to 20V by using Voltmeter. Measure the current I by ammeter for $R=2.2\text{ K}\Omega$ (Use measured values) and record it in the Table 3.
- Turn off the power supply and remove the resistance $2.2\text{ K}\Omega$. Replace it by resistor $3.3\text{ K}\Omega$.
- Now turn on the power supply. Measure and record the current I in turn, at each of the resistance settings shown in the Figure 2.
- Calculate the values of resistance R_T by using $R_T=V/I$. Use measured values of voltage and current.

Physics Laboratory

DATA SHEET:

Table 1: Measuring Resistances by using Ohmmeter


Nominal values of R (K Ω)	Measured values of R (K Ω) by using Ohmmeter	Measured equivalent resistance value of R (K Ω) from circuit
1	0.99	
2.2	2.17	
3.3	3.24	
4.7	4.7	
5.6	5.57	
10	9.74	
$R_s=R_{eq}=R_{nom}=R_T=$	$R_{mes}=$	$R_{eq}=R_{ckt}=$

Table 2: Current versus Voltage reading

Supply Voltage (V)	Measured I by using Ammeter (mA)	$R_T = R_{1K\Omega} + R_{2.2K\Omega}$ [Use measured values of R] (k Ω)	Calculate Current, I $I = V/R_T$ (mA)	Measured Resistance, $R_T = V/I$ (k Ω)
5	1.5		1.58	
10	3			11
15	4.5	3.16	2.16	
20	6		4.74	3.17
25	7.5		6.33	
			7.91	11

Table 3: Current versus Resistance reading

Supply Voltage (V)	Measured I by using Ammeter (mA)	R_T [Use measured values of R] (K Ω)	Resistance, $R_T = V/I$ (K Ω)
20	6	$R_T = R_{1K} + R_{2.2K}$	3.33
		$R_T = 3.16$	
20	4.5	$R_T = R_{1K} + R_{33K}$	4.4
		$R_T = 4.23$	
20	3	$R_T = R_{1K} + R_{47K}$	6.6
		$R_T = 5.63$	
20	2.5	$R_T = R_{1K} + R_{56K}$	8
		$R_T = 6.56$	
20	1.8	$R_T = R_{1K} + R_{10K}$	11.11
		$R_T = 10.73$	

Signature of the Teacher

Discussions:

Q: What can you say about the relationship between the voltage and current, provided that the resistance is fixed?

From ohm's law we get $V = IR$. If R is fixed then we can write $V \propto I$. That is to say, with increase of supplied voltage the current flowing through the circuit will increase and with the decrease of supplied voltage value of current will also decrease.

Q: Plot a graph of I versus V keeping the value of resistance constant. Use measured values of I and V . Comment on the graph briefly.

$$\tan \theta \frac{dx}{dy} = \text{slope} \Rightarrow \frac{I}{V} = \frac{y}{x} = \frac{6-3}{20-10} = 0.3 \text{ mA/V}$$

$$R = \frac{V}{I} = \frac{5}{1.6} = 3.125 \text{ k}\Omega$$

$$R_{\text{graph}} = 3.3 \text{ k}\Omega$$

$$R_{\text{measured}} = 3.17 \text{ k}\Omega$$

The graph will be straight line. In all case proves $V = IR$

Q: Plot a graph of I versus R_T keeping the value of supply voltage constant. Use measured values of I and R_T .

Comment on the graph briefly.

We know, $V = IR$

$$\begin{aligned} \therefore V_1 &= I_1 R_1 \\ &= 6.4 \times 3.17 \\ &= 20.28 \end{aligned}$$

$$\begin{aligned} V_2 &= 4.5 \times 4.23 \\ &= 19.04 \end{aligned}$$

$$\begin{aligned} V_3 &= 3 \times 5.69 \\ &= 17.07 \end{aligned}$$

$$V_4 = 2.5 \times 6.56 = 16.4$$

$$V_5 =$$

$$\therefore V_g = \frac{V_1 + V_2 + V_3 + V_4}{4}$$

$$\therefore V_{\text{graph}} = 18.18$$

$$V_{\text{supply}} =$$